

Analysis of the model from a mathematical point of view


Let's consider the first elementary circuit with which we can schematize the axon.

To determine the trend of the potential and currents we use Kirchooff's laws:

$$V_{smax} = V_{r_i} + V_C$$

and

$$i_i = i_c + i_m$$

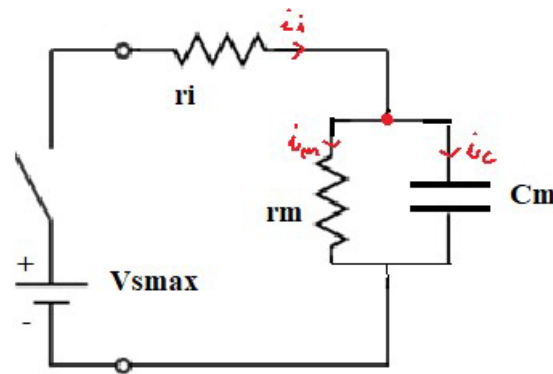

where V_{smax} is the potential across the RC circuit that we imagine as the d.d.p of a generator, V_{r_i} is the ddp across the internal resistance of the axon and V_C is the d.d.p ai Condenser C ends. By i_m we also indicate the current through the membrane.

We derive i_c and express everything as a function of the potentials:

$$i_m = \frac{V_C}{r_m}, \quad i_i = \frac{V_{smax} - V_C}{r_i}, \quad i_c = i_i - i_m$$

so what

$$i_c = \frac{V_{smax} - V_C}{r_i} - \frac{V_C}{r_m}$$

Since the following relation holds for a capacitor:

$$V_C = \frac{q}{c_m}$$

we will have

$$i_c = \frac{V_{smax}}{r_i} - \frac{q}{r_i c_m} - \frac{q}{r_m c_m}$$

Deriving the previous expression with respect to time, we obtain:

$$\frac{di_c}{dt} = -\left(\frac{1}{r_i} + \frac{1}{r_m}\right) \frac{i_c}{c_m}$$

which is a linear differential equation with separable variables whose solution is obtained by integrating:

$$\int \frac{di_c}{i_c} = -\left(\frac{1}{r_i} + \frac{1}{r_m}\right) \frac{1}{c_m} \int dt$$

$$i_c(t) = Ae^{-\frac{t}{\tau}}$$

The time constant τ is

$$\tau = \frac{r_i r_m c_m}{r_i + r_m}$$

The constant A is determined by the initial conditions of the circuit.

For

$$t=0 \quad i_c(0) = A = i_i(0) = \frac{V_{smax}}{r_i}$$

and then

$$i_c(t) = \frac{V_{smax}}{r_i} e^{-\frac{t}{\tau}}$$

Usually $r_m \sim 104 \, \Omega/m$ and $r_i \sim 1010 \, \Omega\mu$ and r_m can be neglected compared to r_i , which allows to simplify τ :

$$\tau = \frac{r_i r_m c_m}{r_i + r_m} \sim r_m c_m$$

We then find the other currents as a function of time:

$$i_m(t) = \frac{V_c}{r_m} = \int \frac{i_c(t)}{r_m c_m} dt$$

The solution is:

$$i_m(t) = \frac{V_{smax}}{r_i + r_m} \left(1 - e^{-\frac{t}{\tau}}\right)$$

In the end

$$i_i(t) = i_c(t) + i_m(t) = \frac{V_{smax}}{r_i + r_m} \left(1 + \frac{r_m}{r_i} e^{-\frac{t}{\tau}}\right)$$

For $t=0$ all the current passes through the resistor r_i and goes to charge the capacitor c_m . No current circulates through r_m , $i_m(0) = 0$, in accordance with the fact that it is in parallel with c_m and has no d.d.p. at its ends.


For long times, ($t \rightarrow \infty$) the capacitor is charged and no longer circulates current through the branch i.e. $i_c(\infty) = 0$, while all the current passes through the internal and membrane resistance:

$$i_i(\infty) = i_m(\infty) = \frac{V_{smax}}{r_i + r_m}$$


The expressions found analytically for currents justify a result that we had previously introduced, namely the stimulus potential:

$$V_s(t) = V_{smax}(1 - e^{-\frac{t}{\tau}})$$

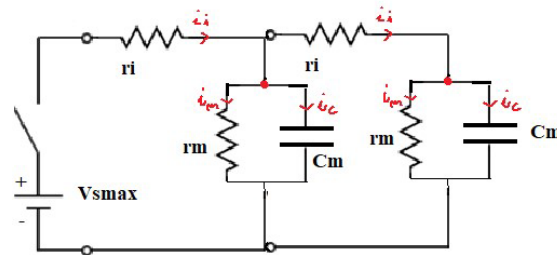To simulate the axon, we consider other similar circuits connected to the first. For this second circuit, the potential or f.e.m. is no longer V_{smax} but the potential present to the heads of the parallel


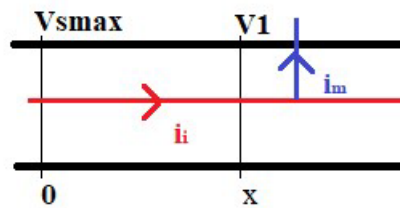
$$V_c = i_m r_m = \frac{V_{smax} r_m}{r_i + r_m} \sim \frac{r_m}{r_i} V_{smax}$$



The stimulus potential decreases along the axon.

Let us consider the stimulus potential V_{smax} at the point $x=0$. Its propagation depends on the current flowing within axon II, which in turn depends (according to Ohm's first law) on the variation of potential along the axon:

$$i_i(x) = -\frac{1}{r_i} \frac{dV_s}{dx}$$

The minus sign depends on the fact that the current flows from points to higher potentials points with lower potentials, then in the opposite direction to the gradient of V_s . The internal current decreases because the charges flow out of the membrane via the current i_m :

$$\frac{di_i}{dx} = -i_m = -\frac{V_s}{r_m}$$

Substituting we get the following second-order differential equation:

$$V_s = -r_m \frac{di_i}{dx} = \frac{r_m}{r_i} \frac{d^2 V_s}{dx^2}$$

The solution is:

$$V_s(x) = V_{smax} e^{-\frac{x}{\lambda}}$$

with

$$\lambda = \sqrt{\frac{r_m}{r_i}}$$

as we had previously introduced.